

Practice Problem (2)

Design an electronic lock system (**lockSys**, see Figure 1) for a garage door lock. The electronic lock accepts a 3-digit user code input, one digit at a time. If the input code sequence exactly matches 010, the electronic lock is opened (**openLock** is asserted). If any part of the 3-digit code input sequence is incorrect, the **Alarm** is activated and the user is forced to restart code entry i.e. all backward arcs go back to the initial state if a "wrong" digit is entered. When **openLock** is asserted after the correct code has been entered, the lock stays open. And the lock shuts itself (**openLock** is de-asserted) if the asynchronous input signal **rst** is asserted or a 0/1 is entered after the correct input code sequence, until the correct input code is again entered.


 


Figure 1. Electronic Lock System (lockSys)

- (a) Design a Mealy/Moore FSM for **lockSys**.
- (b) Implement the FSM in (a) in Verilog.

Solution:

(a)

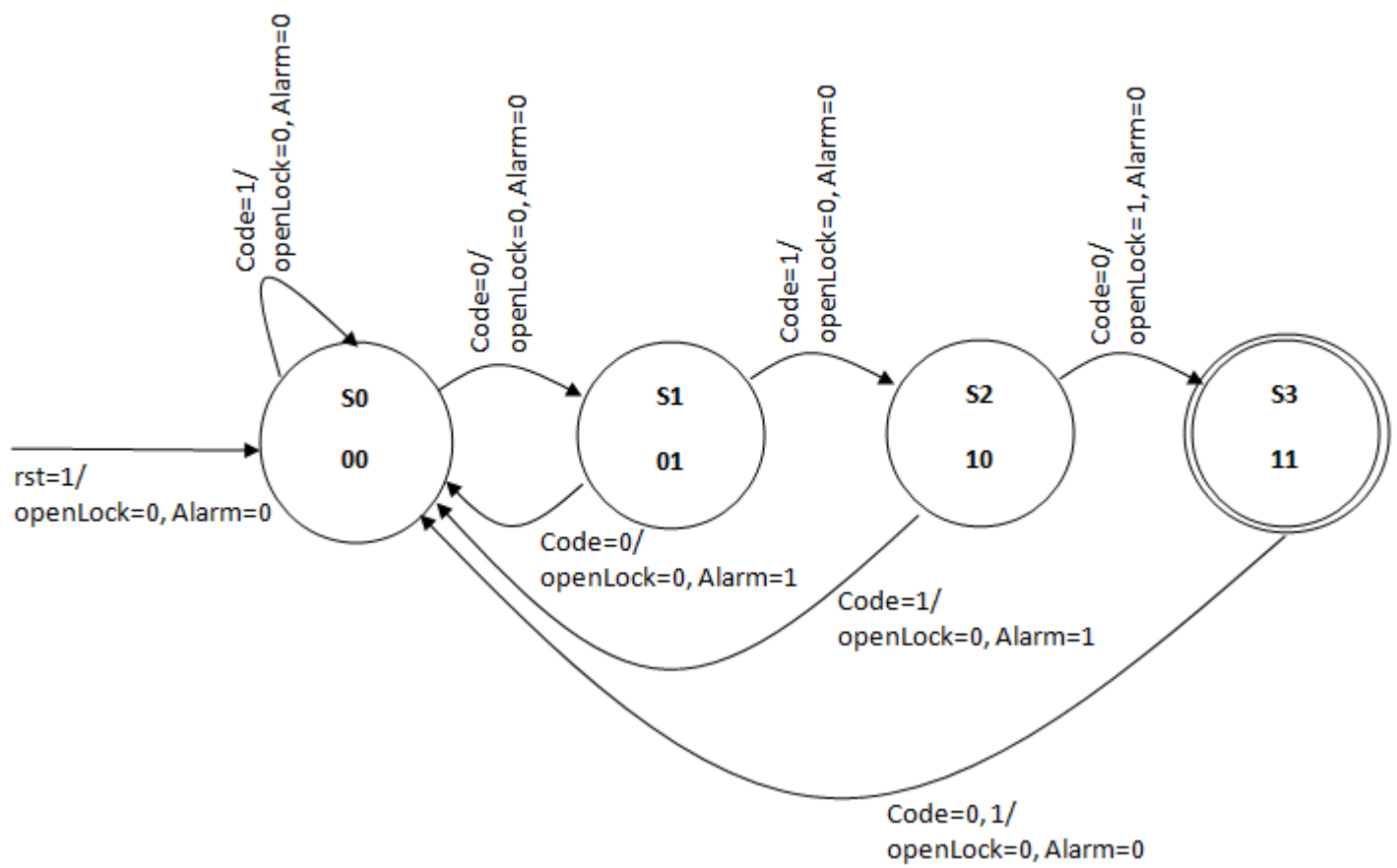

(b)

```
module sysLock (Code, clk, rst, openLock, Alarm);

    input Code, clk, rst;
    output openLock, Alarm;
    reg openLock, Alarm;

    parameter S0 = 0, S1 = 1, S2 = 2, S3 = 3;
    reg [1:0] state;

    always @(posedge clk, rst)
        if (rst) begin
            openLock <= 0;
            Alarm <= 0;
            state <= S0;
        end
        else
            case (state)
                S0: begin
                    openLock = Code?0:0;
                    Alarm = Code?0:0;
                    state = Code?S0:S1;
                end
                S1: begin
                    openLock = Code?0:0;
                    Alarm = Code?0:1;
                    state = Code?S2:S0;
                end
                S2: begin
                    openLock = Code?0:1;
                    Alarm = Code?1:0;
                    state = Code?S0:S3;
                end
                S3: begin
                    openLock = Code?0:0;
                    Alarm = Code?0:0;
                    state = Code?S0:S0;
                end
            endcase
endmodule
```

```

module tst_sysLock;

    reg Code, clk, rst;
    wire openLock, Alarm;

    sysLock lock (Code, clk, rst, openLock, Alarm);

    initial    begin
        clk = 0;
        #10 Code = 1;
        #20 Code = 0;
        #20 Code = 1;
        #20 Code = 0;
        #20 Code = 1;
        #20 Code = 0;
        #20 Code = 0;
        #20 Code = 1;
        #20 Code = 0;
        #20 Code = 1;
        #20 Code = 0;
    end

    initial    begin
        rst = 1;
        #10 rst = 0;
    end

    always
        #10 clk = ~clk;

endmodule

```

