

LAB 4
INTRODUCTION TO XILINX ISE AND Spartan 6 BOARD and
implementation of MUX and DECODERS



Spring 2025

Submitted by: **Mohsin Sajjad**

Registration No: **22pwsce2149**

Class Section: **A**

“On my honor, as student of University of Engineering and Technology, I have neither given
nor received unauthorized assistance on this academic work.”

A handwritten signature in black ink that reads "Mohsin Sajjad".

Student Signature: _____

Submitted to:

Engr. Faheem Jan

Month Day, Year (16 03, 2025)

Department of Computer Systems Engineering
University of Engineering and Technology, Peshawar

Objectives:

- Introduction to FPGA
- Introduction Xilinx ISE

Lab Task:

Task 01:

Develop a program to control on Board LED using On board available switch.

Code:

```
18 // Additional Comments:
19 //
20 ///////////////////////////////////////////////////////////////////
21 module buffer(O,I);
22 input [7:0] I;
23 output [7:0] O;
24 assign O=I;
25 endmodule
```

Output:



Task 02:

Develop a program that implements a 2x1 multiplexer on the board. Connect the inputs to switches and output to led.


Code:

```

20 //////////////////////////////////////////////////
21 module mux2X1(I, sel, out);
22     input [1:0] I; // 2 input lines
23     input sel;     // Selection line
24     output out;
25     assign out = sel ? I[1] : I[0]; // MUX selects I[1] when sel=1, I[0] when sel=0
26 endmodule

```

Output:

 

Task 03:

Develop a program that implements a 4x1 multiplexer on the board. Connect the inputs to switches and output to led.


Code:

```

20 //////////////////////////////////////////////////
21 module mux4x1(I, sel, out);
22     input [3:0] I; // 4 input lines
23     input [1:0] sel; // 2-bit selection line
24     output reg out; // Output declared as reg for procedural assignment
25     always @(*) begin
26         if (sel == 2'b00)
27             out = I[0];
28         else if (sel == 2'b01)
29             out = I[1];
30         else if (sel == 2'b10)
31             out = I[2];
32         else
33             out = I[3];
34     end
35 endmodule

```

Output:

 

Task 04:

Implement 2X4 Decoder and 3x8 Decoder on the Board.

2X4:

Code:

```

20 //////////////////////////////////////////////////
21 module decoder2X4(A, B, D);
22     input A, B;
23     output [3:0] D;
24
25     assign D[0] = ~A & ~B;
26     assign D[1] = ~A & B;
27     assign D[2] = A & ~B;
28     assign D[3] = A & B;
29 endmodule

```

3X8:

Code:

```

20 //////////////////////////////////////////////////
21 module decoder3x8(A, B, C, D);
22     input A, B, C; // 3 input lines
23     output [7:0] D; // 8 output lines
24
25     assign D[0] = ~A & ~B & ~C;
26     assign D[1] = ~A & ~B & C;
27     assign D[2] = ~A & B & ~C;
28     assign D[3] = ~A & B & C;
29     assign D[4] = A & ~B & ~C;
30     assign D[5] = A & ~B & C;
31     assign D[6] = A & B & ~C;
32     assign D[7] = A & B & C;
33 endmodule

```

Output:



Task 05:

Implement NOT gate using MUX

Code:

```
20 ///////////////////////////////////////////////////////////////////
21 module not_using_mux(A, Y);
22     input A;    // Input
23     output Y;   // Output
24
25     assign Y = A ? 1'b0 : 1'b1; // MUX functionality: Y = (A) ? 0 : 1
26 endmodule
```

Output on Xilinx:

