

Digital System Design

Lab01



Spring 2025

Submitted by: **Mohsin Sajjad**

Registration No: **22pwsce2149**

Class Section: **A**

“On my honor, as student of University of Engineering and Technology, I have neither given nor received unauthorized assistance on this academic work.”

A handwritten signature in black ink that reads "Mohsin Sajjad".

Student Signature: _____

Submitted to:

Engr. Faheem Jan

Month Day, Year (16 02, 2025)

Department of Computer Systems Engineering
University of Engineering and Technology, Peshawar

LAB No 1

INTRODUCTION TO MODELSIM AND GATE LEVEL MODELING

Objectives:

Introduction to MODELSIM

Software used:

MODELSIM

MODELSIM:

MODELSIM is a simulator which can be used for the simulations of both VHDL and Verilog HDL. It has the following interface.

TASKS:

1. Implement a buffer at the gate level.

CODE:

```
module buffer(I,O);
  input I;
  output O;
  buf b(O,I);
endmodule

module buffer_tb();
  reg I;
  wire O;
  buffer inst(I,O);
initial begin //for multiple lines
  I=0;
  #20 $display("I = %b",I,"O = %b",O);

  I=1;
  #20 $display("I = %b",I,"O = %b",O);
end
endmodule
```

Truth table:

```
VSIM 4> run
# I = 00 = 0
# I = 10 = 1
```

Wave output:



2. Implement an inverter at the gate level.


Code:

```
Ln# |  
1  | module inverter(I,O);  
2  |     input I;  
3  |     output O;  
4  |     not a(O,I);  
5  | endmodule  
6  |  
7  | module inverter_dut();  
8  |     reg I;  
9  |     wire O;  
10 |     inverter b(I,O);  
11 |     initial  
12 |     begin  
13 |         I=0;  
14 |         #20 $display("I=%b",I,"O=%b",O);  
15 |         I=1;  
16 |         #20 $display("I=%b",I,"O=%b",O);  
17 |     end  
18 | endmodule
```

Truth Table:

```
VSIM 14> run  
# I=0O=1  
# I=1O=0
```

Wave output:

 

3. Implement an OR gate using a NAND gates.

Code:

```
module orgate(A, B, O);
  input A, B;
  output O;
  wire nandout1, nandout2;
  nand n1(nandout1, A);
  nand n2(nandout2, B);
  nand n3(O, nandout1, nandout2);

endmodule

module or_gate();
  reg A, B;
  wire O;
  orgate x(A, B, O);

initial begin
  A = 0; B = 0;
  #20 $display("A = %b, B = %b, O = %b", A, B, O);

  A = 0; B = 1;
  #20 $display("A = %b, B = %b, O = %b", A, B, O);


  A = 1; B = 0;
  #20 $display("A = %b, B = %b, O = %b", A, B, O);

  A = 1; B = 1;
  #20 $display("A = %b, B = %b, O = %b", A, B, O);
end

endmodule
```

```
VSIM 23> run
# A = 0, B = 0, O = 0
# A = 0, B = 1, O = 1
# A = 1, B = 0, O = 1
# A = 1, B = 1, O = 1
```

Wave output:

 

4. Implement the following equation where z is output and x1, x2, x3, x4, and x5 are inputs of the circuit.

$$z = (y1 + y2)'$$

$$y1 = x1.x2$$

$$y2 = (x3.x4.x5)$$

```
module equ(Z,x1,x2,x3,x4,x5);
  input x1,x2,x3,x4,x5;
  output Z;
  wire y1;
  wire y2;
  and n1(y1,x1,x2);
  and n2(y2,x3,x4,x5);
  nor n3(Z,y1,y2);
endmodule

module equ_tb();
  reg x1,x2,x3,x4,x5;
  wire Z;
  equ ins(Z,x1,x2,x3,x4,x5);
  initial begin
    x1=0;
    x2=0;
    x3=0;
    x4=0;
    x5=0;
    #20 $display("x1 = %b",x1, "x2 = %b",x2,"x3 = %b",x3,"x4 = %b",x4,"x5 = %b",x5,"Z = %b",Z);

    x1=0;
    x2=0;
    x3=0;
    x4=0;
    x5=1;
    #20 $display("x1 = %b",x1, "x2 = %b",x2,"x3 = %b",x3,"x4 = %b",x4,"x5 = %b",x5,"Z = %b",Z);

    x1=0;
    x2=0;
    x3=0;
    x4=1;
    x5=0;
    #20 $display("x1 = %b",x1, "x2 = %b",x2,"x3 = %b",x3,"x4 = %b",x4,"x5 = %b",x5,"Z = %b",Z);
  end
endmodule
```


Truth Table:

```
add wave -position insertpoint sim:/equ_tb/*
VSIM 19> run
# x1 = 0x2 = 0x3 = 0x4 = 0x5 = 0Z = 1
# x1 = 0x2 = 0x3 = 0x4 = 0x5 = 1Z = 1
# x1 = 0x2 = 0x3 = 0x4 = 1x5 = 0Z = 1
# x1 = 0x2 = 0x3 = 0x4 = 1x5 = 1Z = 1
```

Wave output:



5.

 

Topic: Simplification

$$Y = \bar{y}_1 + y_2$$

$$y_1 = \bar{a} \cdot x_2$$

$$x_2 = b \cdot x_1$$

$$x_1 = (b \cdot c)$$

$$x_2 = b \cdot (b \cdot c)$$

$$x_2 = b \cdot (b + \bar{c})$$

$$x_2 = b \cdot b + b \cdot \bar{c}$$

$$x_2 = b \cdot \bar{c}$$

$$y_1 = \bar{a} \cdot b \cdot \bar{c}$$

$$y_1 = (\bar{a} \cdot b \cdot \bar{c})$$

$$y_1 = a + b \cdot c$$

$$y_2 = (x_2 \oplus \bar{x}_1)$$

$$y_2 = \bar{x}_1 \cdot x_2 + x_1 \cdot \bar{x}_2$$

$$y_2 = (b \cdot c) \cdot (b \cdot \bar{c}) + (b \cdot c) \cdot (b \cdot \bar{c})$$

$$y_2 = (b \cdot c) \cdot (b + \bar{c}) + (b \cdot \bar{c}) \cdot (b \cdot \bar{c})$$

$$y_2 = (b \cdot c \cdot b) + (b \cdot \bar{c} \cdot c) + (b \cdot \bar{c} \cdot b) + (b \cdot \bar{c} \cdot \bar{c})$$

$$y_2 = a + (b \cdot c) + (b \cdot \bar{c}) + (b \cdot \bar{c})$$

$$y_2 = (b \cdot c) + (b \cdot \bar{c})$$

$$y_2 = b(c + \bar{c})$$

$$y_2 = b \cdot 1$$

$$y_2 = b$$

So

$$Y = a + b \cdot c + b \Rightarrow a + c + b + \bar{b}$$

$$Y = a + c + 1 = 1$$

```

module logic_circuit(output Y, input A, B, C):
    wire A_not, X1, X2, X2_not, Y1, Y2, Y1_not;

    // Inverters
    not n1(A_not, A);
    not n2(X1_not, X1);

    // AND Gates
    nand a2(X1,B, C);
    and a3(X2,X1,B);
    and a1(Y1, A_not, X2);
    // XOR Gate
    xor x1(Y2, X2, X1_not);

    // Inverter for Y1
    not n3(Y1_not, Y1);

    // OR Gate
    or o1(Y, Y1_not, Y2);
endmodule

module logic_circuit_tb():
    reg A, B, C;
    wire Y;
    logic_circuit uut(Y, A, B, C);

    initial begin
        // Display header
        $display("A B C | Y");
        $display("-----");

        // Test all possible input combinations
        A = 0; B = 0; C = 0; #10; $display("%b %b %b | %b", A, B, C, Y);
        A = 0; B = 0; C = 1; #10; $display("%b %b %b | %b", A, B, C, Y);
        A = 0; B = 1; C = 0; #10; $display("%b %b %b | %b", A, B, C, Y);

        A = 0; B = 1; C = 0; #10; $display("%b %b %b | %b", A, B, C, Y);
        A = 0; B = 1; C = 1; #10; $display("%b %b %b | %b", A, B, C, Y);
        A = 1; B = 0; C = 0; #10; $display("%b %b %b | %b", A, B, C, Y);
        A = 1; B = 0; C = 1; #10; $display("%b %b %b | %b", A, B, C, Y);
        A = 1; B = 1; C = 0; #10; $display("%b %b %b | %b", A, B, C, Y);
        A = 1; B = 1; C = 1; #10; $display("%b %b %b | %b", A, B, C, Y);

        $stop;
    end
endmodule

```

Truth table:

```

VSIM 27> run
# A B C | Y
# -----
# 0 0 0 | 1
# 0 0 1 | 1
# 0 1 0 | 1
# 0 1 1 | 1
# 1 0 0 | 1
# 1 0 1 | 1
# 1 1 0 | 1
# 1 1 1 | 1
# ** Note: $stop : D:/Semester
# Time: 80 ns Iteration: 0

```

Wave output:

