

Lab 10

A Digital Lock



Spring 2025

Submitted by: **Mohsin Sajjad**

Registration No: **22pwsce2149**

Class Section: **A**

“On my honor, as student of University of Engineering and Technology, I have neither given nor received unauthorized assistance on this academic work.”

A handwritten signature in black ink that reads "Mohsin Sajjad". The signature is written in a cursive, flowing style.

Student Signature: _____

Submitted to:

Engr. Faheem Jan


Month Day, Year (18 05, 2025)

Department of Computer Systems Engineering
University of Engineering and Technology, Peshawar


A Digital Lock

Objective: Build an electronic combination lock with reset button, two number buttons (0 and 1), and an unlock output. The combination should be “01011”

Block Diagram: A combinational digital lock has three input buttons for Reset, entering a “0” and entering a “1” and output button UNLOCK and state which shows in which state the machine is currently in. The state output is connected to the seven segment display on the S6BOARD. The Module button in the below diagram is an abstraction of the synchronizer and level to pulse converter from the previous lab. The state transition diagram is given in the following figures.

 

State Transition Diagram:

 

Lab Tasks:

- 1- Build an electronic combination lock with reset button, two number buttons (0 and 1), and an unlock output. The combination should be "01011"

CODE:

```
module Lock(button0, button1, clk_in, rst, openLock, PS);
```

```
    input button0, button1, clk_in, rst;
```

```
    output openLock;
```

```
    output reg [2:0]PS;
```

```
    reg openLock;
```

```
    parameter    S0 = 3'b000,
```

```
                S1 = 3'b001,
```

```
S2 = 3'b010,
```

```
S3 = 3'b011,
```

```
S4 = 3'b100,
```

```
S5 = 3'b101;
```

```
reg [2:0] state;
```

```
wire slowclock;
```

```
Clock_Divider cd(clk_in, slowclock);
```

```
always @(posedge slowclock) begin
```

```
    if (rst) begin
```

```
        openLock = 0;
```

```
        state = S0;
```

```
    end else begin
```

```
        case (state)
```

```
            S0: begin
```

```
                if (!button0)    // input 0
```

```
                    state = S1;
```

```
                else if (!button1)
```

```
                    state = S0;
```

```
            end
```

```
            S1: begin
```

```
    if (!button1)    // input 1 => 01
        state = S2;
    else if (!button0)
        state = S1;
end
```

```
S2: begin
    if (!button0)    // input 0 => 010
        state = S3;
    else if (!button1)
        state = S0;
end
```

```
S3: begin
    if (!button1)    // input 1 => 0101
        state = S4;
    else if (!button0)
        state = S1;
end
```


```
S4: begin
    if (!button1)    // input 1 => 01011
        state = S5;
    else if (!button0)
```

```
        state = S1;
    end


    S5: begin
        // Once unlocked, reset or wait for reset
        if (!button0 || !button1)
            state = S0;
        end
    endcase
end

PS <= state;

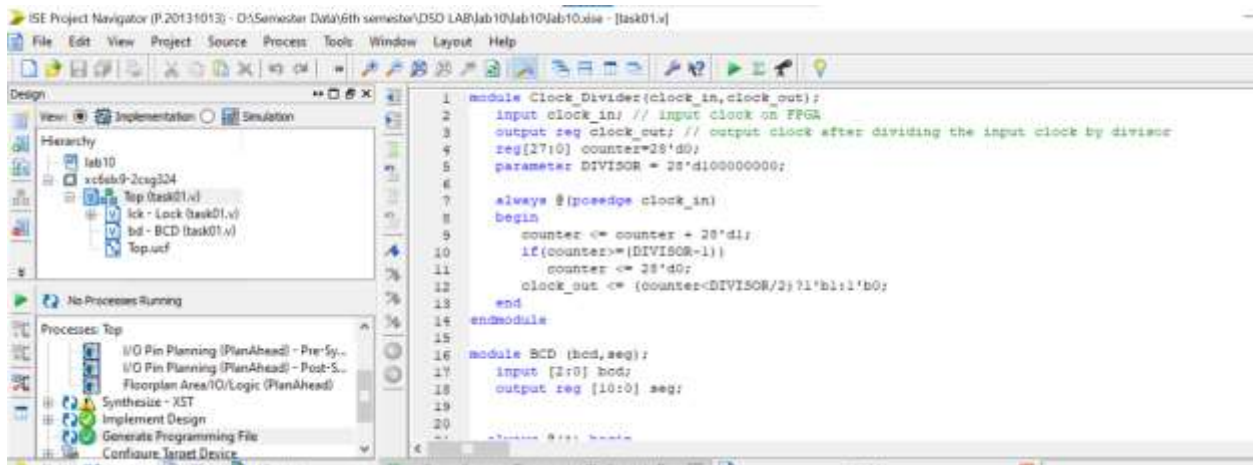if (state == S5)
    openLock = 1;
else
    openLock = 0;
end
endmodule
```



output:

 

Conclusion:

This Verilog code implements a digital lock system that unlocks when the button sequence **01011** is entered. It uses a finite state machine (FSM) to track the input pattern, a clock divider to slow down the clock, and a 7-segment display module to show the current FSM state. When the correct sequence is entered, the `Unlock` output goes high.

TASK 02:

Change the functionality of the lock such that it unlocks on the sequence of 11011.

CODE:

```
module Clock_Divider(clock_in,clock_out);

    input clock_in; // input clock on FPGA

    output reg clock_out; // output clock after dividing the input clock by divisor

    reg[27:0] counter=28'd0;

    parameter DIVISOR = 28'd100000000;

    always @(posedge clock_in)
    begin
        counter <= counter + 28'd1;

        if(counter>=(DIVISOR-1))
            counter <= 28'd0;

        clock_out <= (counter<DIVISOR/2)?1'b1:1'b0;
    end

endmodule

module BCD (bcd,seg);
```



```

        input [2:0] bcd;

        output reg [10:0] seg;


always @(*) begin

    case(bcd)

        3'b000: seg = 11'b100000000011; // 0

        3'b001: seg = 11'b11110010011; // 1

        3'b010: seg = 11'b01001000011; // 2

        3'b011: seg = 11'b01100000011; // 3

        3'b100: seg = 11'b00110010011; // 4

        3'b101: seg = 11'b00100100011; // 5


        default: seg = 11'b00000000011; // Error or Blank A

    endcase

end


endmodule


module Lock(button0, button1, clk_in, rst, openLock, PS);

    input button0, button1, clk_in, rst;

    output openLock;

    output reg [2:0]PS;

    reg openLock;

```

```
parameter          S0 = 3'b000,

                  S1 = 3'b001,

                  S2 = 3'b010,

                  S3 = 3'b011,

                  S4 = 3'b100,

                  S5 = 3'b101;

reg [2:0] state;

wire slowclock;

    Clock_Divider (clk_in,slowclock);

always @(posedge slowclock) begin

    if (rst) begin

        openLock = 0;

        state = S0;

    end

    else begin

        case (state)

S0: begin

            if (!button1) // first 1
```

```
        state = S1;

    else if (!button0)

        state = S0;

end
```

S1: begin

```
    if (!button1) // second 1 ? 11

        state = S2;

    else if (!button0)

        state = S0;

end
```

S2: begin

```
    if (!button0) // zero ? 110

        state = S3;

    else if (!button1)

        state = S0;

end
```

S3: begin

```
    if (!button1) // fourth 1 ? 1101

        state = S4;

    else if (!button0)
```

```

        state = S0;

    end

S4: begin
    if (!button1) // fifth 1 ? 11011
        state = S5;
    else if (!button0)
        state = S0;
    end

S5: begin
    if (!button1)
        state = S0;
    else if (!button0)
        state = S0;
    end
endcase

end //else

    PS <= state;

    if(PS==S5)
        openLock = 1;
    else

```

```
openLock = 0;
```

```
end                                     // always end
```

```
endmodule
```

```
module Top(BT0, BT1, clk, rst, Unlock, seg);
```

```
    input BT0, BT1, rst, clk;
```

```
    output Unlock;
```


```
    wire [2:0]PS;
```

```
    output [10:0] seg;
```


```
    Lock lck(BT0, BT1, clk, rst, Unlock, PS);
```

```
    BCD bd(PS,seg);
```

```
endmodule
```

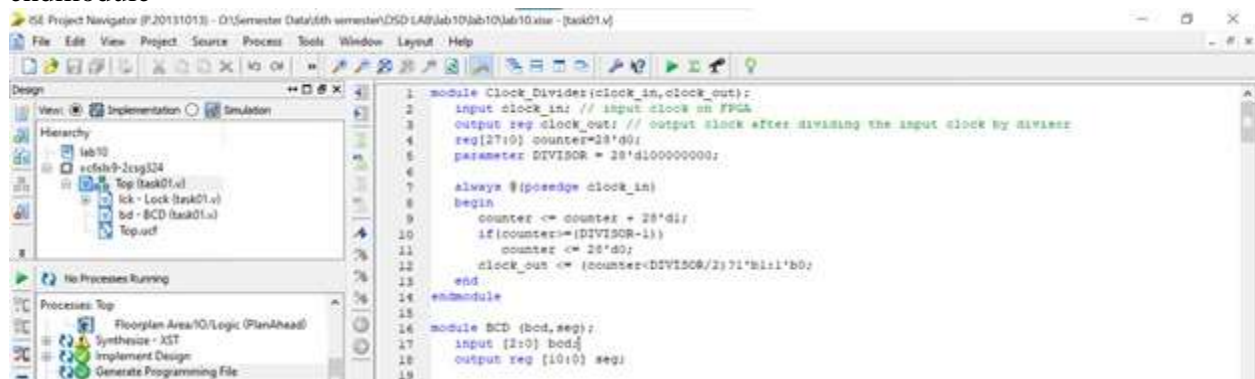

Output:

 

Conclusion:

This Verilog code implements a digital lock system that unlocks when the button sequence 01011 is entered. It uses a finite state machine (FSM) to track the input pattern, a clock divider to slow down the clock, and a 7-segment display module to show the current FSM state. When the correct sequence is entered, the `Unlock` output goes high.