

## Lab 08

### 4 digit BCD Counter on Multiplexed Seven Segment Display



**Spring 2025**

Submitted by: **Mohsin Sajjad**

Registration No: **22pwsce2149**

Class Section: **A**

“On my honor, as student of University of Engineering and Technology, I have neither given nor received unauthorized assistance on this academic work.”

A handwritten signature in black ink, which appears to read "Mohsin Sajjad".

Student Signature: \_\_\_\_\_

Submitted to:

**Engr. Faheem Jan**


Month Day, Year (04 05, 2025)

Department of Computer Systems Engineering  
University of Engineering and Technology, Peshawar

## 4 digit BCD Counter on Multiplexed Seven Segment Display
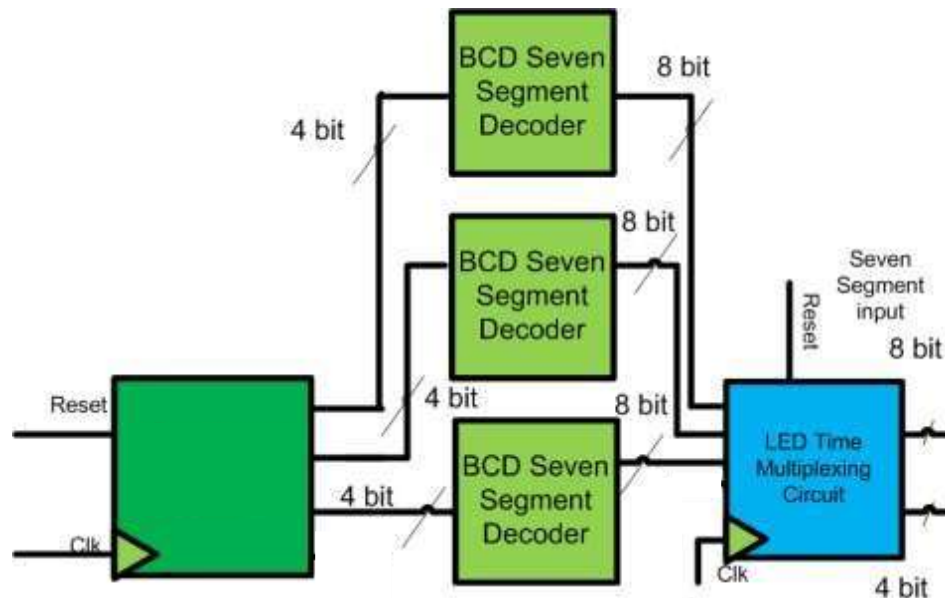
### Objective:

Learn to use time multiplexed 4 digit Seven Segment display



### Lab Task:

Implement a BCD counter that runs from 000 to 999 and shows each BCD digit on the seven segment display.

### CODE:

// BCD Counter

```
module BCD_Counter (input CLOCK, input CLR, output reg [3:0] Q);
```

```
    always @(negedge CLOCK or posedge CLR) begin
```

```
        if (CLR)
```

```
            Q <= 4'd0;
```

```
        else if (Q == 4'd9)
```

```
            Q <= 4'd0;
```

```
        else
```

```
            Q <= Q + 1;
```

```
    end
```

```
endmodule
```

// Three BCD Counters (unit, ten, hundred)

```

module three_BCD(input CLOCK, input CLR, output [3:0] BCDu, BCDt, BCDh);

    wire tc_u, tc_t;

    BCD_Counter bcd_u(CLOCK, CLR, BCDu);

    BCD_Counter bcd_t(BCDu[3], CLR, BCDt);

    BCD_Counter bcd_h(BCDt[3], CLR, BCDh);

endmodule

```

#### // BCD to 7 Segment

```

module BCD_to_7seg(input [3:0] bcd, output reg [7:0] seg);

    always @(*) begin

        case (bcd)

            4'b0000: seg = 8'b11000000; // 0

            4'b0001: seg = 8'b11111001; // 1

            4'b0010: seg = 8'b10100100; // 2

            4'b0011: seg = 8'b10110000; // 3

            4'b0100: seg = 8'b10011001; // 4

            4'b0101: seg = 8'b10010010; // 5

            4'b0110: seg = 8'b10000010; // 6

            4'b0111: seg = 8'b11111000; // 7

            4'b1000: seg = 8'b10000000; // 8

            4'b1001: seg = 8'b10010000; // 9

            default: seg = 8'b11111111; // error

        endcase

    end

endmodule

```

#### // Clock Divider

```

module Clock_Divider(input clock_in, output reg clock_out);

    reg [27:0] counter = 28'd0;

    parameter DIVISOR = 28'd100000000; // Adjust according to FPGA clock

    always @(posedge clock_in) begin

        if (counter == DIVISOR-1) begin

```

```

        counter <= 28'd0;

        clock_out <= ~clock_out;

    end else begin

        counter <= counter + 1;

    end

end

endmodule

```

#### // 18-bit Counter

```

module Counter18bit(input clk, input rst, output reg [17:0] count);

    always @(posedge clk or posedge rst) begin

        if (rst)

            count <= 18'd0;

        else

            count <= count + 1;

        end

    endmodule

```

#### // 4X1 Multiplexer

```

module mux4X1(

    input [7:0] bcd0,

    input [7:0] bcd1,

    input [7:0] bcd2,

    input [1:0] select,

    output reg [7:0] out

);

    always @(*) begin

        case(select)

            2'b00: out = bcd0;

            2'b01: out = bcd1;

            2'b10: out = bcd2;

            default: out = 8'b11111111; // blank

        endcase

    end

end

```

Like someone **\*\*clapping very fast\*\*** — 100 million claps per second.

But you only want to turn on a light once per second**\*\***.

So, you:

1. Count the claps.
2. When you've counted enough (say 100 million),
3. You flip a switch (turn the light ON if it was OFF, or OFF if it was ON).
4. Then you start counting again.

This way, even though claps are fast, you slow things down using **\*\*counting\*\***.

Now in Verilog:

```

reg [27:0] counter = 0; // a big number to
count fast clock pulses
```

```

This is your clap counter.

It increases every time the FPGA clock ticks.

```

if (counter == DIVISOR-1) begin
    counter <= 0;
    clock_out <= ~clock_out; // flip the output
    signal
end
```

```

If the counter reaches the target (like 100 million), flip `clock\_out`.

Reset the counter to start counting again.

```
endmodule
```

#### // 2X4 Decoder

```
module decoder2X4(  
    input [1:0] select,  
    output reg [3:0] out  
);  
    always @(*) begin  
        case(select)  
            2'b00: out = 4'b1110;  
            2'b01: out = 4'b1101;  
            2'b10: out = 4'b1011;  
            2'b11: out = 4'b0111;  
        endcase  
    end  
endmodule
```

#### // Top Module

```
module topMultiplexer(  
    input clk,  
    input rst,  
    output [3:0] out_dec,  
    output [7:0] out_mux  
);  
    wire slow_clock;  
    wire [3:0] BCDu, BCDt, BCDh;  
    wire [7:0] bcd1, bcd2, bcd3;  
    wire [17:0] counter_out;  
  
    Counter18bit cnt(clk, rst, counter_out);  
    Clock_Divider divider(clk, slow_clock);  
  
    three_BCD three_BCD_Counters(slow_clock, rst, BCDu, BCDt, BCDh);  
    BCD_to_7seg B1(BCDu, bcd1);
```





```
BCD_to_7seg B2(BCDt, bcd2);
```

```
BCD_to_7seg B3(BCDh, bcd3);
```


```
mux4X1 Mux(bcd1, bcd2, bcd3, counter_out[17:16], out_mux);
```

```
decoder2X4 d1(counter_out[17:16], out_dec);
```

```
endmodule
```

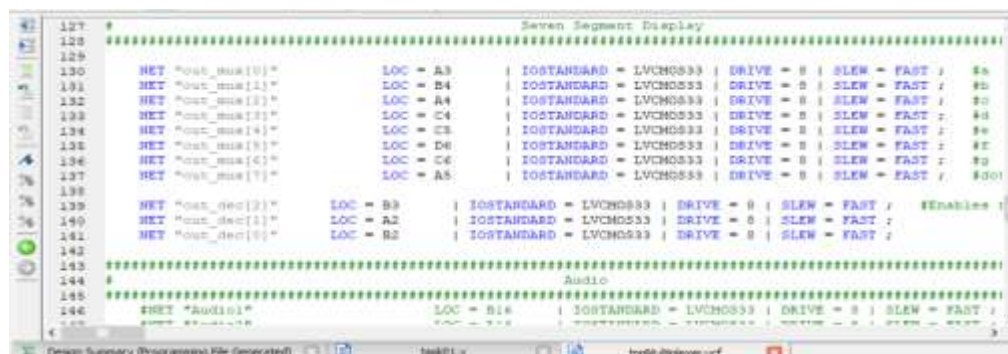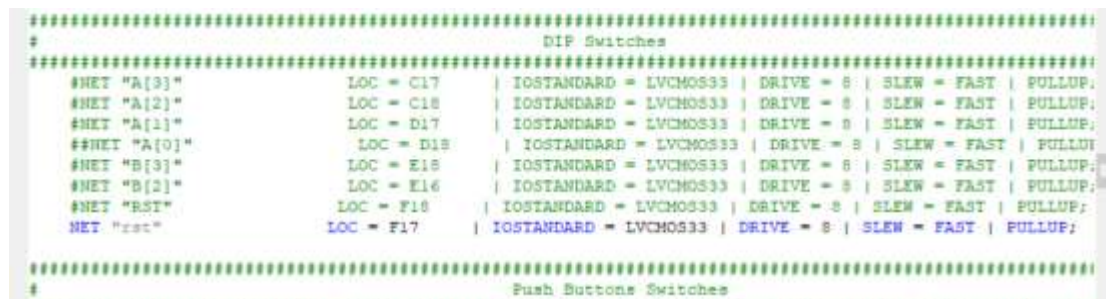 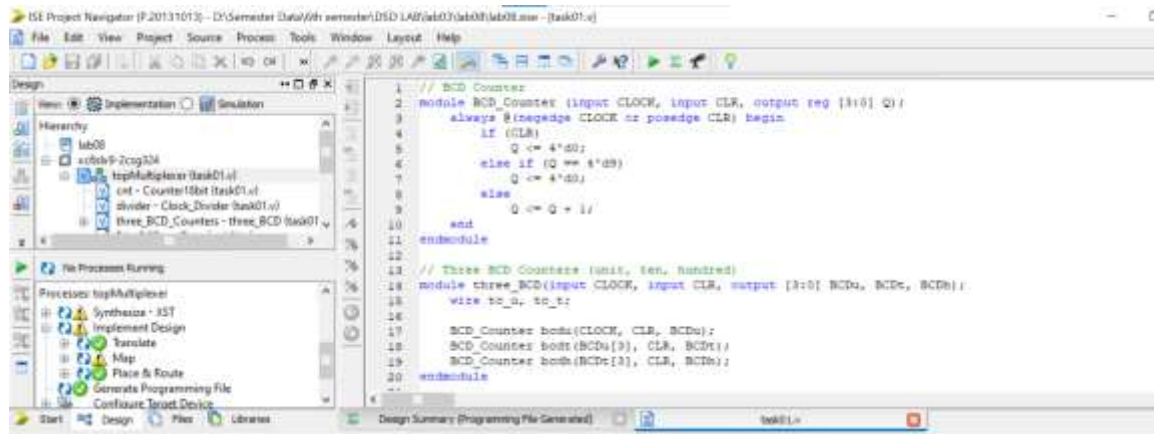

## OUTPUT:

 

## Conclusion:

We implements a digital BCD counter system with display functionality. It includes a chained three-digit BCD counter for units, tens, and hundreds, each displayed on a 7-segment display. A clock divider and an 18-bit counter manage timing and multiplexing of displays. The `mux4X1` selects which BCD digit to show, while the `decoder2X4` activates the corresponding display. This design demonstrates modular digital design using counters, decoders, multiplexers, and display drivers. It is ideal for learning and implementing multi-digit BCD counting and display systems in FPGAs.